

## Lecture 15 - Isolated DC-DC converters

Often, the output DC voltage from a DC-DC converter must be isolated from the input AC supply. DC power supplies for appliances and equipment are good examples. It is advantageous to have the isolation transformer on the DC side, where the switching frequency is high.

### 1. Isolation


Transformer isolation at the AC side is bulky.


### 2. Multiple Outputs

Multiple isolated outputs possible, using one high frequency core.
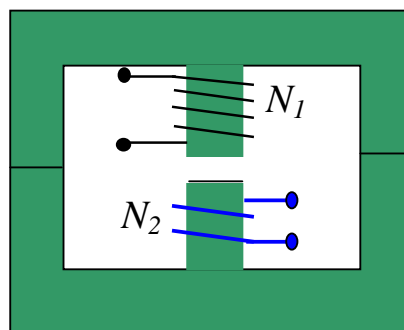
### 3. Regulation (PWM duty cycle $D$ -control) can take advantage of the transformer ratio.

DC side transformer allows design flexibility by making the range of  $D$  more suitable.



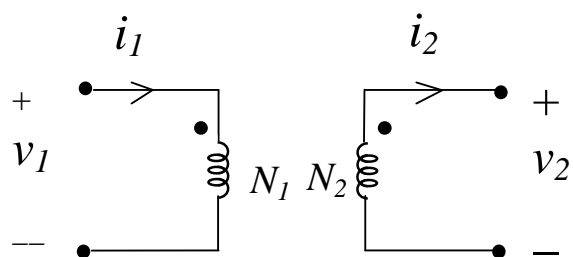

$$V_1/N_1 = V_2/N_2 ; \quad I_1 N_1 = I_2 N_2$$

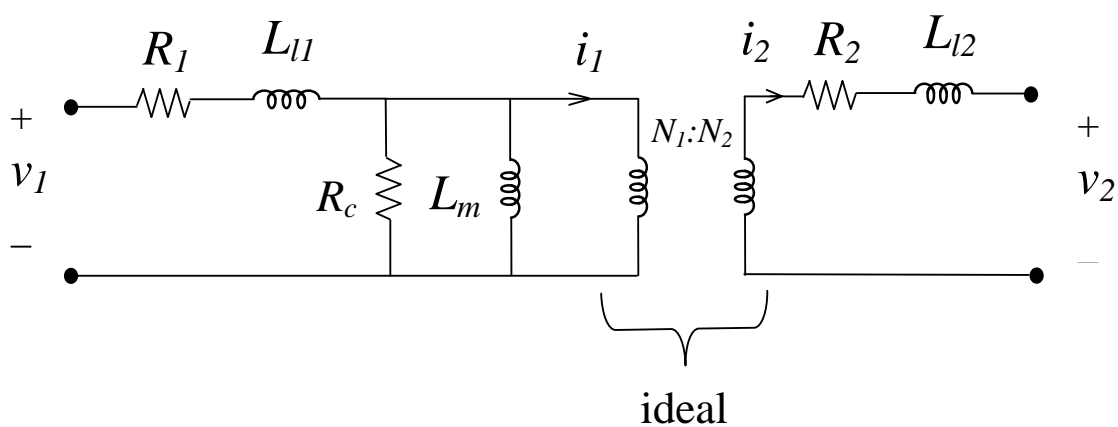


Figure 15.1(a)

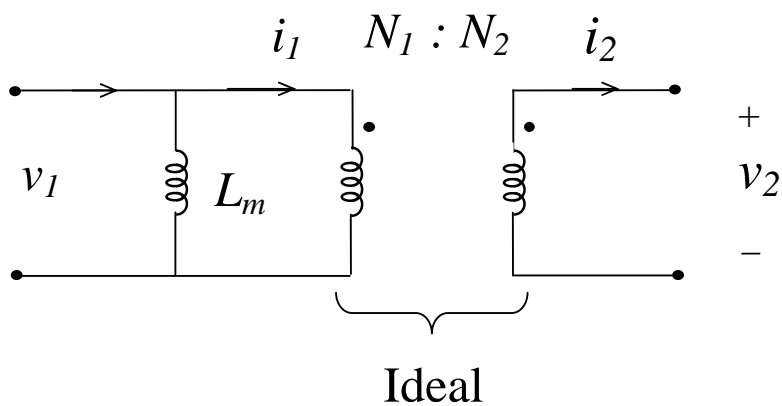


Figure 15.1 (b)

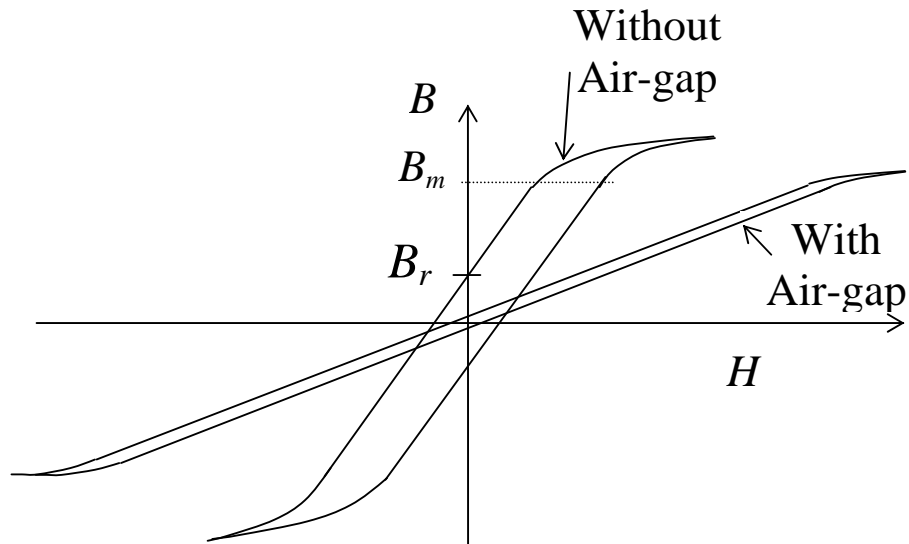


Figure 15.2

The airgap reduces the  $B_r$ , which is the  $B$  when  $i_m$  (or  $H_c$ ) falls to zero. In a converter, this minimizes the snubber components which would be required to reset the core flux in each switching cycle. Operation with flux reset increases the range of variation of the flux in the core thereby increasing the utilization of the transformer (or reducing its size).

- **Unidirectional core excitation**

Flyback (buck-boost derived) and Forward (buck derived) converters

- **Bidirectional core excitation**




Push-pull, half-bridge and full-bridge converters

$L_1, L_2$  must be as small as possible for power loss considerations of the switches.


$L_m$  must be as large/small as practicable from energy storage considerations.  $L_m$  should be large for forward converters, small for flyback converters.

### **Space for Figures on magnetic materials**
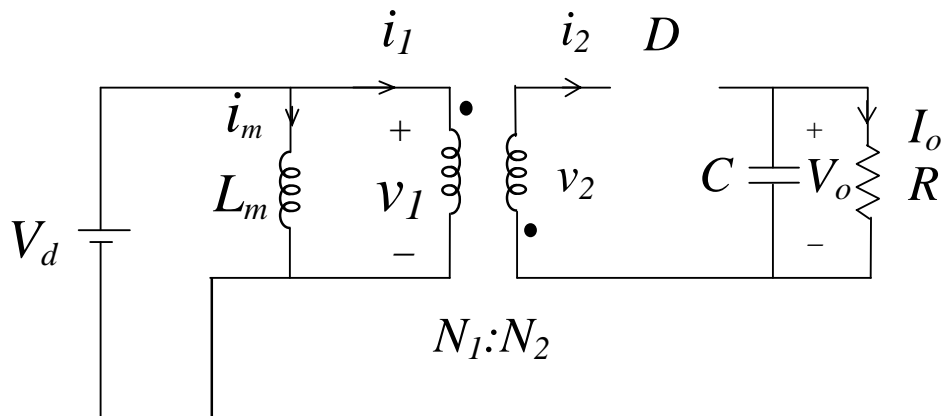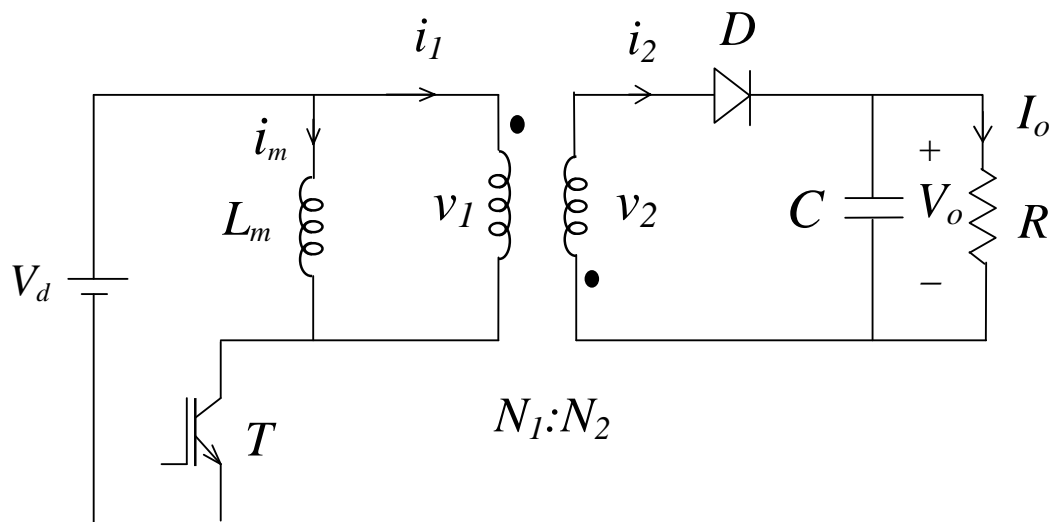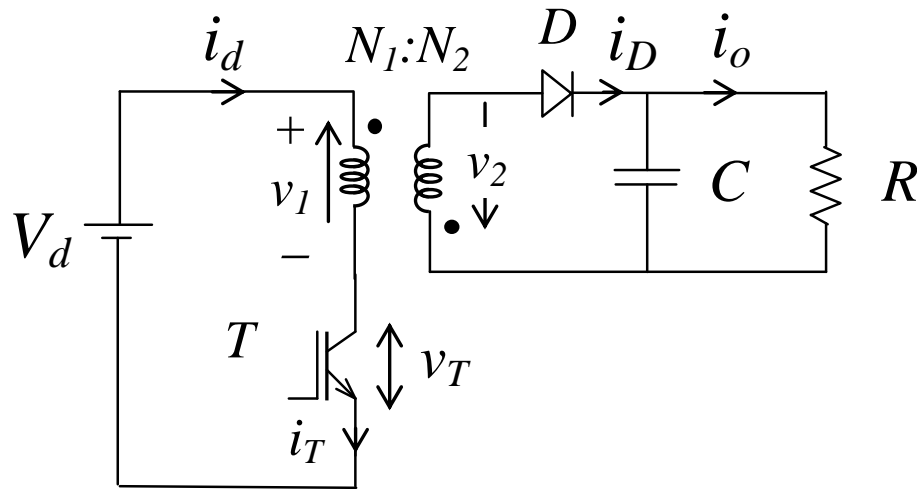
# Flyback Converter (Derived from the Buck-Boost Converter)



Circuit during  $t_{on}$  ;  $v_1 = V_d$

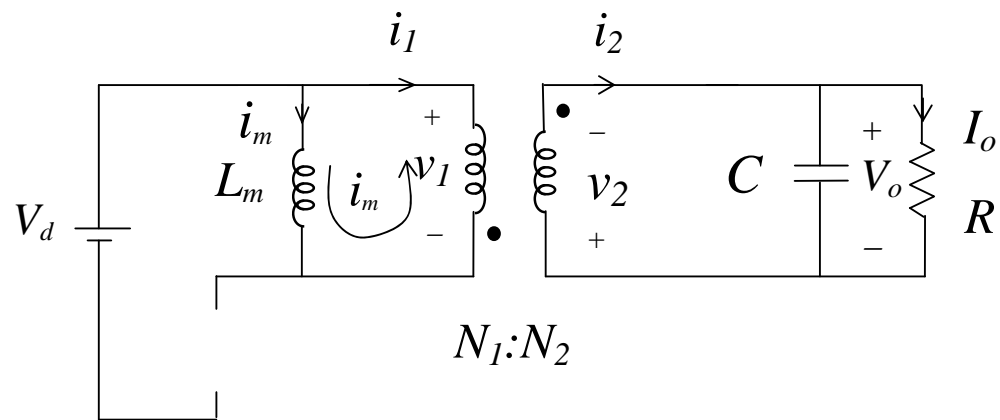

Circuit during  $t_{off}$  ;  $i_2 = i_D$

Figure 15.3

# Analysis of the Flyback converter

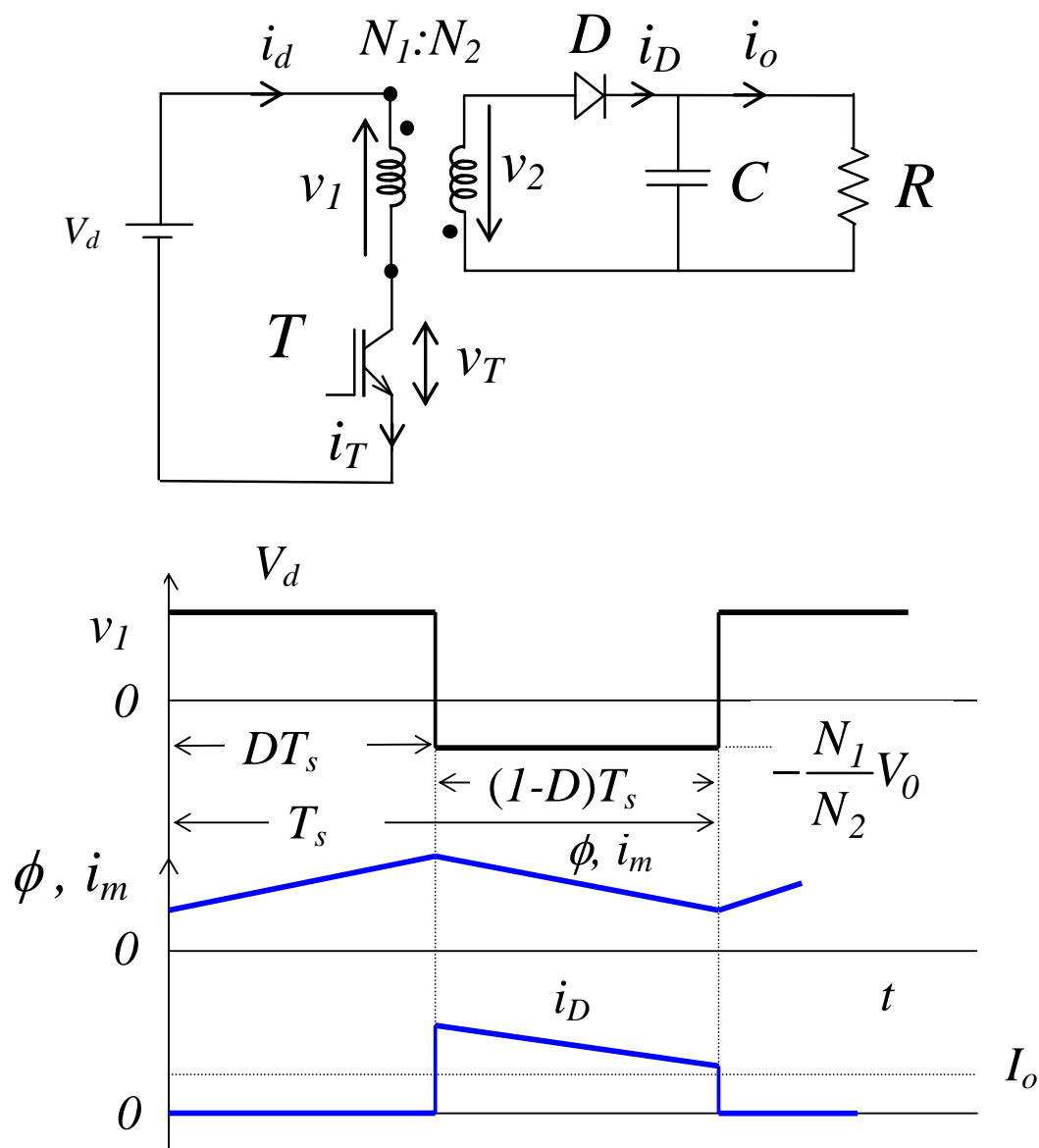


Figure 15.4

$$v = N \frac{d\phi}{dt} \quad \text{or} \quad \frac{v}{N} = \frac{d\phi}{dt} \quad (15.1)$$

During  $0 < t < t_{on}$ , for the primary side,

$$\phi = \phi_0 + \frac{I}{N_1} \int_0^t V_d dt \quad (15.2)$$

$$\phi(t_{on}) = \phi_0 + \frac{V_d}{N_1} t_{on} = \phi_0 + \frac{V_d}{N_1} D T_s = \phi_{max} \quad (15.3)$$

During  $t_{on} < t < T_s$  for the secondary side,

$$-V_o = N_2 \frac{d\phi}{dt} \quad (15.4)$$

$$\therefore -\frac{I}{N_2} \int_{t_{on}}^t V_o dt = \phi_{max} - \frac{V_o}{N_2} (t - t_{on}) \quad (15.5)$$

$$\phi(T_s) = \phi_{max} - \frac{V_o}{N_2} (T_s - t_{on}) = \phi_0 + \frac{V_d}{N_1} D T_s - \frac{V_o}{N_2} (T_s - t_{on}) \quad (15.6)$$

If  $\phi(0) = \phi(T_s)$

$$\therefore \frac{V_o}{V_d} = \frac{N_2}{N_1} \frac{D}{1-D} \quad (15.7)$$

Note that  $\phi(0)$  should be as small as possible in order to have the highest flux variation possible.

From power balance, 
$$\frac{I_d}{I_o} = \frac{N_2}{N_1} \frac{D}{1-D} \quad (15.8)$$



## Analysis for continuous conduction

From  $v = L \frac{di}{dt}$

During  $0 < t < t_{on}$ ,  $i_D = 0$ ,  $\therefore V_d = L_m \frac{di_m}{dt}$  (15.9)

$$\therefore i_m = i_T = \int_0^{t_{on}} \frac{V_d}{L_m} dt = i_{mmin} + \frac{V_d}{L_m} t$$

$$i_{mmax} = i_{mmin} + \frac{V_d}{L_m} t_{on} \quad (15.10a)$$

During  $t_{on} < t < T_s$ ,  $i_T = 0$  and

$$v_1 = -\frac{N_1}{N_2} V_o$$

$$i_m(t) = i_{mmax} - \frac{(N_1/N_2)V_o}{L_m} (t - t_{on}) \quad (15.10b)$$

$$i_D(t) = \frac{N_1}{N_2} i_m = \frac{N_1}{N_2} \left[ i_{mmax} - \frac{(N_1/N_2)V_o}{L_m} (t - t_{on}) \right] \quad (15.11)$$

Note that  $i_D$  or  $i_m$  becomes minimum when  $t = T_s$ . Thus,

$$i_{D\min} = \frac{N_1}{N_2} \left[ i_{m\max} - \frac{(N_1/N_2)V_o}{L_m} (1-D)T_s \right] \quad (15.11a)$$

$$\text{Also, } i_{D\max} = \frac{N_1}{N_2} i_{m\max} \quad (15.11b)$$

$$\text{Now, } I_D = I_o = \frac{i_{D\max} + i_{D\min}}{2} \times \frac{(1-D)T_s}{T_s} \quad (15.11c)$$

From (15.11a-c)

$$\therefore i_{m\max} = i_{T\max} = \frac{N_2}{N_1} \frac{1}{1-D} I_o + \frac{N_1}{N_2} \frac{(1-D)T_s V_o}{2L_m} \quad (15.12)$$

Equation 15.12 specifies  $i_{T\max}$  for a given maximum load ( $I_{o\max}$ ).

## Operation on continuous-discontinuous boundary

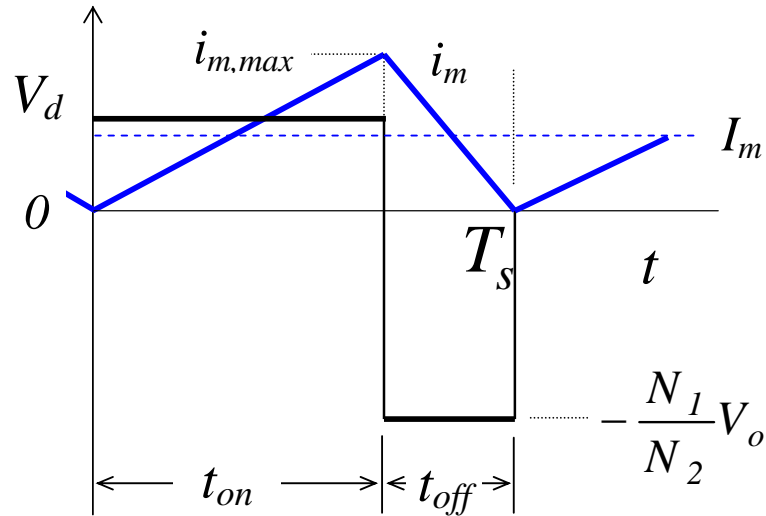


Figure 15.5

$$P_d = P_o \quad \therefore V_d I_d = \frac{V_o^2}{R} \quad (15.13)$$

$$I_d = \frac{I_m D T_s}{T_s} = I_m D \quad (15.14)$$

where  $I_m$  is the average magnetizing current.

$$\therefore V_d I_m D = \frac{V_o^2}{R} \quad \text{so that} \quad I_m = \frac{V_o^2}{V_d R D} \quad (15.15)$$

And

$$I_m = \frac{V_o^2}{V_d R D} = \frac{V_d D}{(1-D)^2 R} \left( \frac{N_2}{N_1} \right)^2 = \frac{V_o}{(1-D) R} \left( \frac{N_2}{N_1} \right) \quad (15.16)$$

$$\therefore i_{m,max} = I_m + \frac{\Delta i_m}{2} = \frac{V_d D}{(1-D)^2 R} \left( \frac{N_2}{N_1} \right)^2 + \frac{V_d D T_s}{2L_m} \quad (15.17)$$

$$i_{m,min} = \frac{V_d D}{(1-D)^2 R} \left( \frac{N_2}{N_1} \right)^2 - \frac{V_d D T_s}{2L_m} \quad (15.18)$$

$$\therefore L_m f_s |_{min} \leq \frac{(1-D)^2 R}{2} \left( \frac{N_1}{N_2} \right)^2 \quad (15.19)$$

to ensure discontinuous conduction. Note that discontinuous conduction of  $i_m$  ensures the largest flux variation in the core of the transformer.

## Flyback converter under discontinuous conduction

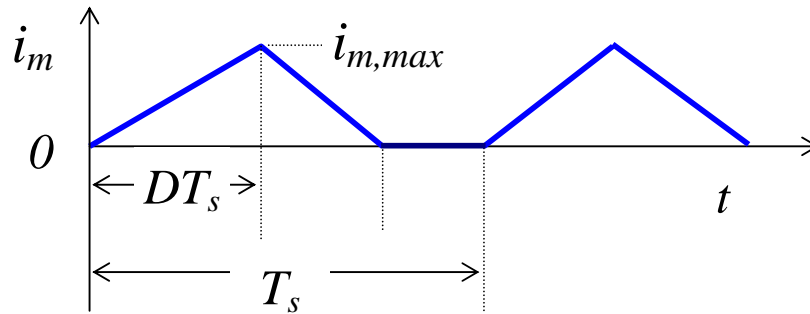


Figure 15.6

$$i_{m \max} = \frac{V_d D T_s}{L_m}$$

$$V_d I_d = \frac{V_o^2}{R} \quad (15.20)$$

$$I_d = \frac{1}{2} \frac{V_d D T_s}{L_m} D T_s / T_s \quad (15.21)$$

$$= \frac{V_d D^2 T_s}{2 L_m} \quad (15.22)$$

$$\therefore V_d I_d = \frac{V_d^2 D^2 T_s}{2 L_m} = \frac{V_o^2}{R} \quad (15.23)$$

$$\therefore \frac{V_o}{V_d} = D \sqrt{\frac{T_s R}{2 L_m}}$$

$$= D \times \sqrt{\frac{R}{2f_s L_m}} \quad (15.24)$$

$$\therefore D = \frac{V_o}{V_d} \sqrt{\frac{2f_s L_m}{R}} \quad (15.25)$$

**Switch voltage,  $v_T$ , during  $t_{on} < t < T_s$**

$$\begin{aligned} v_T &= V_d + \frac{N_1}{N_2} V_o \\ &= V_d + \frac{N_1}{N_2} \frac{N_2}{N_1} \frac{D}{1-D} V_d = \frac{V_d}{1-D} \end{aligned} \quad (15.26)$$

Note: Operation in discontinuous mode utilizes the transformer better. Snubber requirement is also the lowest.

### Output voltage ripple

$$\frac{\Delta V_o}{V_o} = \frac{D}{RCf_s} \quad (15.26)$$

as for a buck-boost converter, assuming continuous conduction. For discontinuous conduction,  $\Delta V_o$  will be worse than this because the output capacitor will lose charge for longer than  $t_{on}$ .

## Two-switch Flyback converter

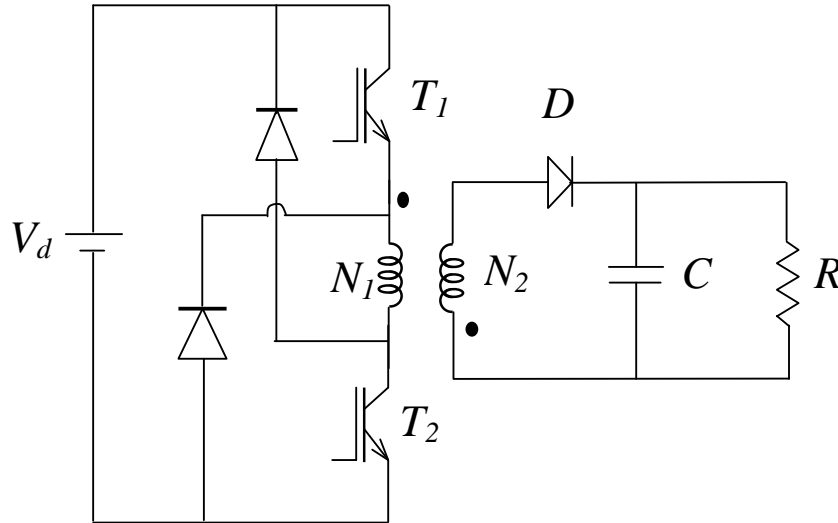


Figure 15.7

- Transistors  $T_1$  and  $T_2$  are turned on and off simultaneously.
- Energy trapped in the leakage inductances now has a regenerative path to flow through. Trapped energies in these inductances return to the DC source.
- Snubber requirement is thus even smaller.
- The two transistors may have half the voltage rating of the single-transistor Flyback converter.