

## Lecture 16 - Forward converters

### Forward Converter (Derived from Buck Converter)

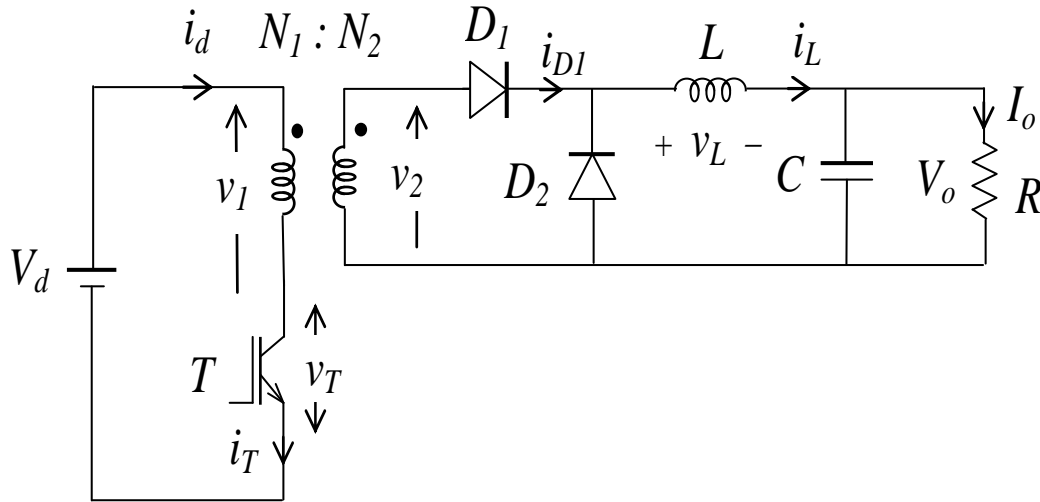


Figure 16.1

During  $0 < t < t_{on}$  :  $D_2$  is reverse biased (i.e., OFF),  $D_1$  is forward biased (i.e., ON) and

$$v_L = \frac{N_2}{N_1} V_d - V_o \quad (16.1)$$

During  $t_{off}$  i.e.,  $t_{on} < t < T_s$  :  $D_1$  is reverse biased (i.e., OFF),  $D_2$  is forward biased (i.e., ON) and

$$v_L = -V_o. \quad (16.2)$$

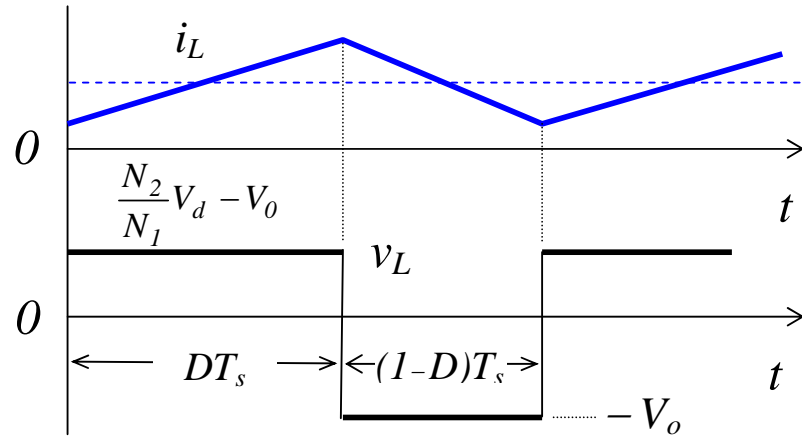


Figure 16.2

$$\frac{\frac{N_2}{N_1} V_d - V_o}{L} DT_s - \frac{V_o}{L} (1 - D) T_s = 0 \quad (16.3)$$

$$\therefore \frac{V_o}{V_d} = \frac{N_2}{N_1} D \quad (16.4)$$

Note that the minimum value of inductor  $L$  for continuous conduction can be found in the same way as for the buck converter (see earlier analysis).

$$I_L = I_o = \frac{V_o}{R} \quad (16.5)$$

$$\Delta i_L = \frac{\left( \frac{N_2}{N_1} \right) V_d - V_o}{L} DT_s \quad (16.6)$$

$$\begin{aligned}
\therefore i_{Lmin} &= I_L - \frac{\Delta I_L}{2} = \frac{V_o}{R} - \frac{\frac{N_2}{N_1} \times \frac{N_1 V_o}{N_2 D} - V_o}{2L} DT_s \\
&= \frac{V_o}{R} - \frac{V_o(1-D)T_s}{2L}
\end{aligned} \tag{16.7}$$

Therefore, for operation at the boundary between continuous and discontinuous conduction, the minimum value of  $L$  is given by,

$$Lf_s|_{\min} = \frac{(1-D)R}{2} \tag{16.8}$$

which is the same formula for the buck converter as found earlier.

The magnetizing current  $i_m$  rises to its maximum value at  $t_{on}$ . Even with continuous conduction in  $L$ , the primary current in the transformer, which is  $-i_m$  during  $t_{off}$ , should be brought down to zero before the end of the switching period  $T_s$ . Otherwise flux build up may take place leading to failure of operation. Furthermore, energy trapped in  $L_m$  when the transistor is turned off must have a path to flow. Clearly, for a forward converter, a large  $L_m$ , meaning small air-gap, low magnetizing current and low energy storage in  $L_m$  is preferred.

## Forward converter with demagnetizing winding and energy return diode

The purpose of the third winding of turns  $N_3$  and the energy return diode  $D_3$  is to return the trapped energy in  $L_m$  at the end of  $t_{on}$  to the DC source. This also helps reset the transformer core flux quickly.

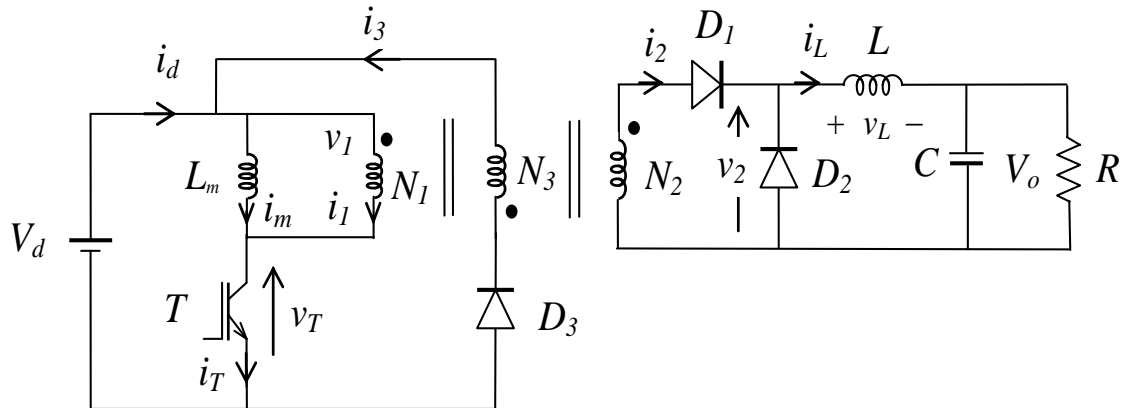


Figure 16.3

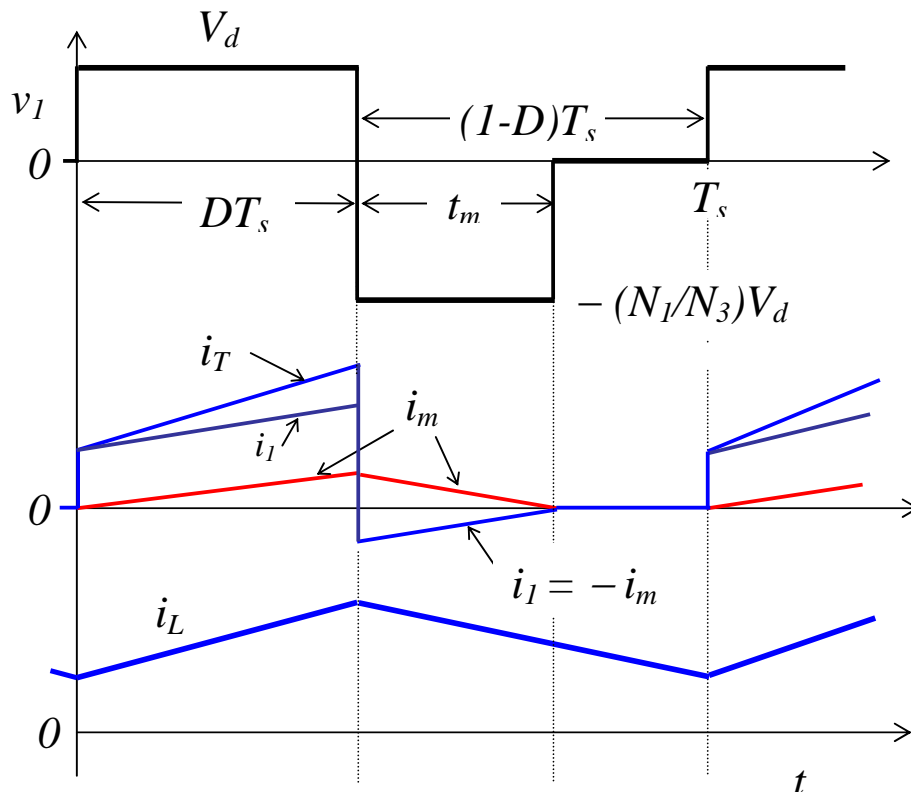


Figure 16.4

### Operation with core flux reset

$$\text{For } 0 < t < t_{on} \quad V_L = V_d \quad (16.9)$$

$$\text{For } t_{on} < t < T_s \quad i_L = -i_m \quad (16.10)$$

For the three-winding transformer

$$N_1 i_L + N_3 i_3 = N_2 i_2 \quad (16.11)$$

During  $t_{off}$ ,  $i_{DL} = i_2 = 0$

$$\therefore i_3 = \frac{N_1}{N_3} i_m \quad (16.12)$$

We assume that during  $t_{off}$ ,  $i_m$  falls to zero in time  $t_m < (1 - D)T_s$ . During  $t_m$ ,

$$\therefore v_L = -\frac{N_1}{N_3} V_d \quad \text{for } t_{on} \leq t \leq (t_{on} + t_m) \quad (16.13)$$

$$\text{From } \int \frac{v_L}{L_m} dt = 0 \quad \text{for } 0 < t < (t_{on} + t_m)$$

$$t_{on} V_d = D T_s V_d = t_m \frac{N_1}{N_3} V_d \quad (16.14)$$

$$\therefore \frac{t_m}{T_s} = \frac{N_3}{N_1} D \quad (16.15)$$

The maximum  $D$  is given by  $t_m = (1 - D_{max})T_s$ , where  $t_m$  is the turn-off time which is available for  $i_m$  to fall to zero.

For any  $D \leq D_{max}$ , complete demagnetization will take place. From (16.11)

$$\therefore (1 - D_{max}) = \frac{N_3}{N_1} D_{max} \quad (16.16)$$

$$\therefore D_{max} = \frac{1}{1 + \frac{N_3}{N_1}} \quad (16.17)$$

If  $N_3 = N_1$ , then  $D_{max} = 0.5$ . Note that

$$v_T = V_d \left( 1 + \frac{N_1}{N_3} \right) \text{ for } t_{on} < t < (t_{on} + t_m) \quad (16.18)$$

$$= V_d \text{ for } (t_{on} + t_m) < t < T_s \quad (16.19)$$

Thus,

- With  $N_3 = N_1$ , if  $D < 0.5$ , the transformer core flux is guaranteed to reset during every cycle.
- Large  $L_m$  makes the demagnetizing winding small. This is in contrast to the Flyback converter for which a small  $L_m$  is good for storing higher energy in  $L_m$  during  $T_{on}$ . Note that the energy stored in  $L_m$  is given by  $\frac{1}{2} L_m i_m^2$ . For the forward converter, the trapped energy in  $L_m$  is not useful.

- Low snubber requirement when the core flux is reset.

## Filter Capacitor

The filter capacitor for the forward converter is given by the same formula as for the buck converter described earlier.

$$\therefore \frac{\Delta V_o}{V_o} = \frac{(1-D)}{8} \frac{T_s^2}{LC} \quad (16.20)$$

## Two-switch Forward converter

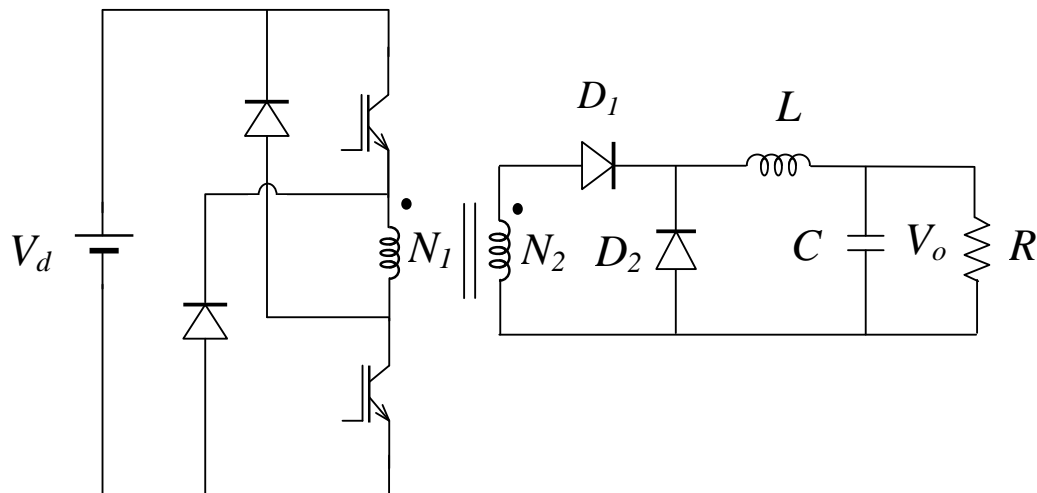


Figure 16.5

In this circuit, the trapped energy in  $L_m$  is returned to the DC source via the two diodes on the input side of the transformer, thus requiring no tertiary (third) winding.